



**Electrical Engineering Department,
Fourth Year - Communications & Electronics.**

EE 431 DIGITAL INTEGRATED CIRCUITS

Lab#1:

Physical Design and Layout of CMOS Inverter

PREPARED BY

Mahmoud Mohamed Kamal Ismail

SECTION

7

SEAT.NO.

250

➤ Contents

1. Screenshot of Layout	Page 2
--------------------------------	---------------

2. Screenshot of netlist (extracted file)	Page 3
--	---------------

3. Screenshot of the Result from simulation	Page 3
--	---------------

➤ List of Figures

Figure 1 Screenshot of Layout	Page 2
--------------------------------------	---------------

Figure 2 No DRC errors	Page 2
-------------------------------	---------------

Figure 3 Screenshot of netlist (extracted file)	Page 3
--	---------------

Figure 4 Screenshot of the Result from simulation	Page 3
--	---------------

1. Screenshot of Layout

 


Figure 1 Screenshot of Layout

 


Figure 2 No DRC errors

2. Screenshot of netlist (extracted file)

```
.include "H:\tanner_l_edit\models\m15_20.mdl"

* Warning: Layers with Unassigned AREA Capacitance.
* <P Base Resistor>
* <Poly Resistor>
* <N Well Resistor>
* <N Diff Resistor>
* <Poly2 Resistor>
* <P Diff Resistor>
* Warning: Layers with Unassigned FRINGE Capacitance.
* <P Base Resistor>
* <Poly1-Poly2 Capacitor>
* <Poly Resistor>
* <N Well Resistor>
* <N Diff Resistor>
* <Poly2 Resistor>
* <P Diff Resistor>
* <Pad Comment>
* Warning: Layers with Zero Resistance.
* <Poly1-Poly2 Capacitor>
* <NMOS Capacitor>
* <PMOS Capacitor>
* <Pad Comment>

* NODE NAME ALIASES

M1 GND IN OUT GND NMOS L=2u W=6u AD=36p PD=24u AS=36p PS=24u
* M1 DRAIN GATE SOURCE BULK (29 19 35 21)
M2 OUT IN VDD VDD PMOS L=2u W=6u AD=36p PD=24u AS=36p PS=24u
* M2 DRAIN GATE SOURCE BULK (29 51.5 35 53.5)
Vin IN GND PULSE (0 5 0 1n 1n 100n 200n)
Vdd VDD GND 5
.tran/powerup 5n 500n method= bdf
.print tran v(IN) v(OUT)
* Total Nodes: 4
* Total Elements: 2
* Total Number of Shorted Elements not written to the SPICE file: 0
* Extract Elapsed Time: 0 seconds
.END
```

Figure 3 Screenshot of netlist (extracted file)

3. Screenshot of the Result from simulation

 


Figure 4 Screenshot of the Result from simulation